Name: Dipesh Digwal

Roll No.: 170121015

Course : PH414(NanoElectronics and NanoPhotonics)

**Exam Number: Open Book Exam 2** 

Date of Submission: 4/11/2020


Nano Sensor Data processor(NSDP) using quantum-dot cellular

### **Objectives**

- Analyse the structure of quantum-dot cellular automata(which is used the represent analogous bits of a classical computer)
- Using the QCA(Quantum-dot cellular automata) as a building blocks for the construction of a simple data processor(4-bit) which can be used in nano sensor data processing
- Compare the traditional MOSFET based data processors with the QCA processor.
 
### **Structure**

**QCA(Quantum-Dot Cellular Automata)**A QCA cell analogous to a MOSFET in operation, contains four quantum dots arranged at the corners of a cube. A QCA cell is given two electrons which by the properties of nanoscale quantum structures to tunnel can change there positions within quantum dots present in a QCA cell in two different ways which are restricted by Coulombic repulsions.




By adjacently joining QCA cells, we get a wire. This wire has a property of transferring information without current flow.

## Methodology
 
#### **QCA Logic Gates**

All logic gates can be reproduced using two gates:

- 3-input majority gate (M(a, b, c) = ab+bc+ac)
- Inverters



Example:

**AND Gate** : AND(a,b) = M(a,b,0) = ab.

**OR Gate** : OR(a, b) = M(a, b, 1) = ab + b · 1 + a · 1 = a + b.

### **Analysis of the processor**

#### **QCA Clocking**

For QCA Clocking we use Adiabatic switching. This switching technique reduces metastability issues and enable deep pipelines.

#### **QCA Design Rules**

#### Layout Design Rules

- 1. Maximum number of cells in single clocking zone: 47 cells
- 2. Minimum number of cells in a single clocking zone: 1 cell (recommended value is 2 cells)
- 3. Minimum wire spacing for signal separation : space of 1 QCA cell
- 4. Wire crossover:
- 5. QCA Equivalent  $\lambda$ -Rule : Single cell size can be used as value of lambda.


#### Timing Design Rules

- 1. Logic Component Timing Rule : For QCA majority gate , inputs from all three input cells should reach centre cell at same time.
- 2. Clocking Zone Assignment Rule: cells in each clocking zone must be synchronised.

#### **NSDP(Nano Sensor Data Processor) Architecture**

Requirements from a NSDP:

 - A. Bridge the preprocessed data which is arriving from sensor to a high-level processor(as in modern computers)
- B. Calculate the population of active majority gates.
- C. Output a approximate sigmoid function which can be directly used processor designed for Artificial neural network(ANN) application.



#### **Preprocessing**


This operation is used to implement majority operation to identify which one from "0" or "1" have majority.

$$m_0 = M(a_0,b_0,c_0),$$

$$m_1 = M(a_1,b_1,c_1),$$

$$m_2 = M(a_2,b_2,c_2),$$

$$m_3 = M(a_3,b_3,c_3)$$

 


This operation takes 3/4 clock cycles to complete.

#### Counter

Two Output terminals from Preprocessing unit are fed to M-latch and Counter subunits. Output of this subunit is given by the formula

$$s_2s_1s_0 = m_3 + m_2 + m_1 + m_0$$

 


### Decoder

Output of this unit is given by

$$f_1 = s_2 s_1,$$


$$f_2 = s_2 s_1 s_0,$$

$$f_3 = s_2 s_1 s_0,$$

 

$$f_4 = s_2 s_1 s_0$$

#### **Pattern Generator**

 


### **Sigmoid Function Output**

$$g_3 = f_{4a} + f_{3a} + f_{2a} + f_{1a},$$

$$g_2 = f_{4b} + f_{3b} + f_{2b} + f_{1b},$$
 
$$g_1 = f_{4c} + f_{3c} + f_{2c} + f_{1c}$$




$$g_0 = f_{4d} + f_{3d} + f_{2d} + f_{1d}$$

#### **Function Control**

$$s_{00} = c_1 c_0$$
,

$$s_{01} = c_1 c_0$$
,

$$s_{10} = c_1 c_0$$
.

 

#### **Output**

This is decided by the appropriate control signals to control unit. This output can be either of the three subunits implemented above ,i.e,


- · Raw majority data
- · Number of active majority gates
- Sigmoid function

$$o_3 = m_3 s_{00} + 0 \cdot s_{01} + g_3 s_{10}$$

$$o_2 = m_2 s_{00} + s_2 \cdot s_{01} + g_2 s_{10},$$

$$o_1 = m_1 s_{00} + s_1 \cdot s_{01} + g_1 s_{10},$$
 
$$o_0 = m_0 s_{00} + s_0 \cdot s_{01} + g_0 s_{10}$$
.



# **Applications**

- Nanosensor data processing
- QCA based error detection circuit

### **Conclusion**

- Alternative structure of classical computers building blocks was analysed.
- NSDP construction is rigorously analysed.
- Wire length and timing of the circuits using QCA vary drastically than MOSFET based classical bits.

## References

 Fenghui Yao, Mohamed Saleh Zein-Sabatto, Guifeng Shao, Mohammad Bodruzzaman and Mohan Malkani, Nanosensor Data Processor in Quantum-Dot Cellular Automata, Journal of Nanotechnology, 2014, 2